

Lab 07

Pre-Lab

Draw the Bode plots for the following circuits. Calculate the corner frequency f_{3dB} , then choose a good scale range, label the axes, then draw the plot.

