


$f_{3dB} (1)$

$V_{out} = 2.5 \text{ squares } (5 \text{ mV}) = 12.5 \text{ mV}$

$V_{in} = 3 \text{ squares } (5 \text{ mV}) = 15 \text{ mV}$

$$\frac{V_{out}}{V_{in}} = \frac{5}{6} \sim 0.707 = 1/\sqrt{2} = -3\text{dB}$$

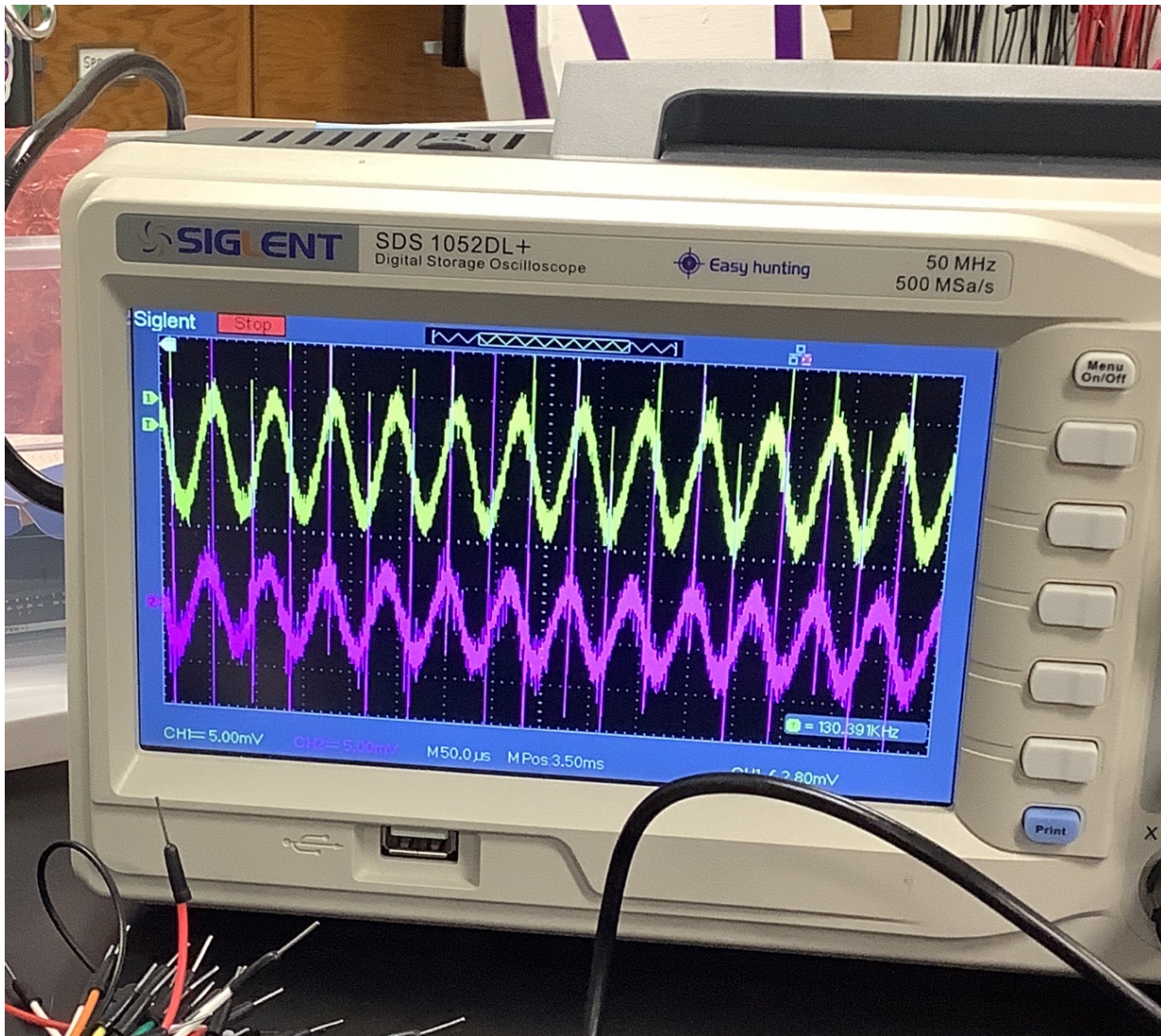Phase shift of $V_{out} \sim -1/8$ of a period = -45 degrees



$$\underline{f_{3dB} \left(\frac{1}{10} \right)}$$


$$V_{out} = 5.4 (100 \text{ mV}) = 540 \text{ mV}$$

$$0.55 (1 \text{ V}) = 0.55 \text{ V}$$

$$V_{in} = 5 (1 \text{ V}) = 5 \text{ V}$$

$$\frac{V_{out}}{V_{in}} = \frac{0.55}{5} = \underline{0.11}$$

phase shift ~ -90 degrees

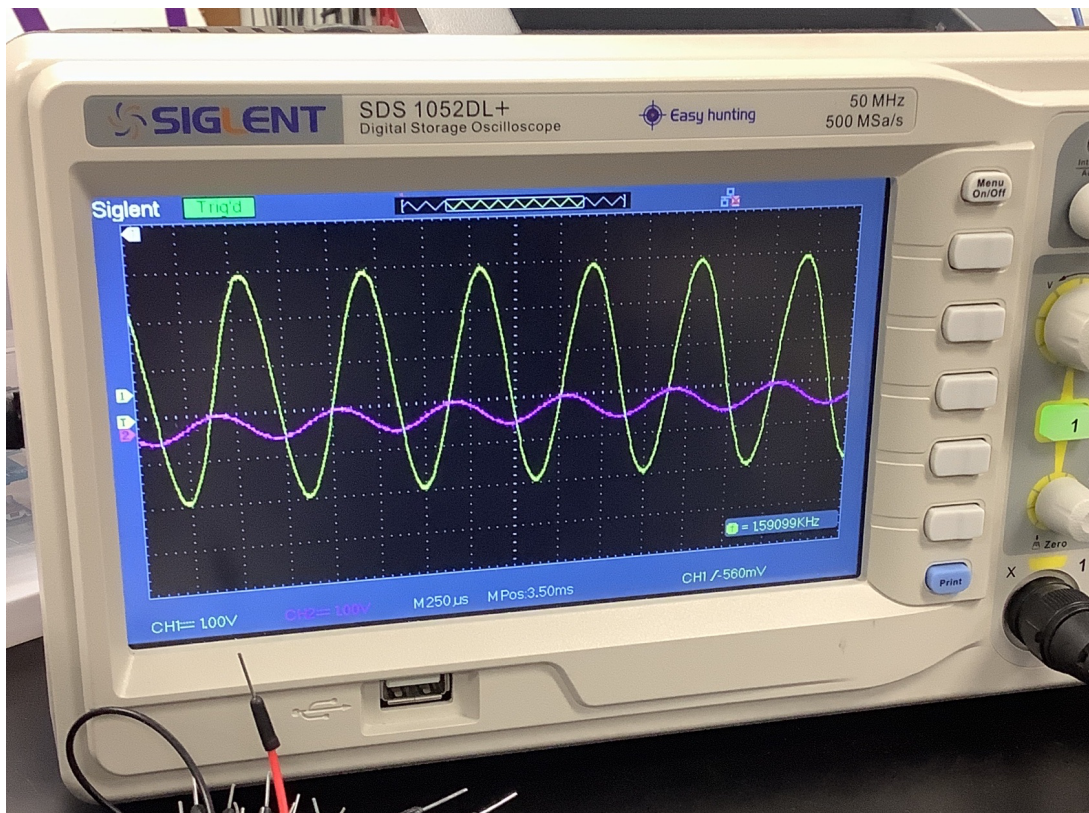


$f_{3dB}(10)$

$V_{out} = 4.4V$

$V_{in} = 4.8V$


$$\frac{V_{out}}{V_{in}} = \frac{4.4}{4.8} = \frac{11}{12}$$

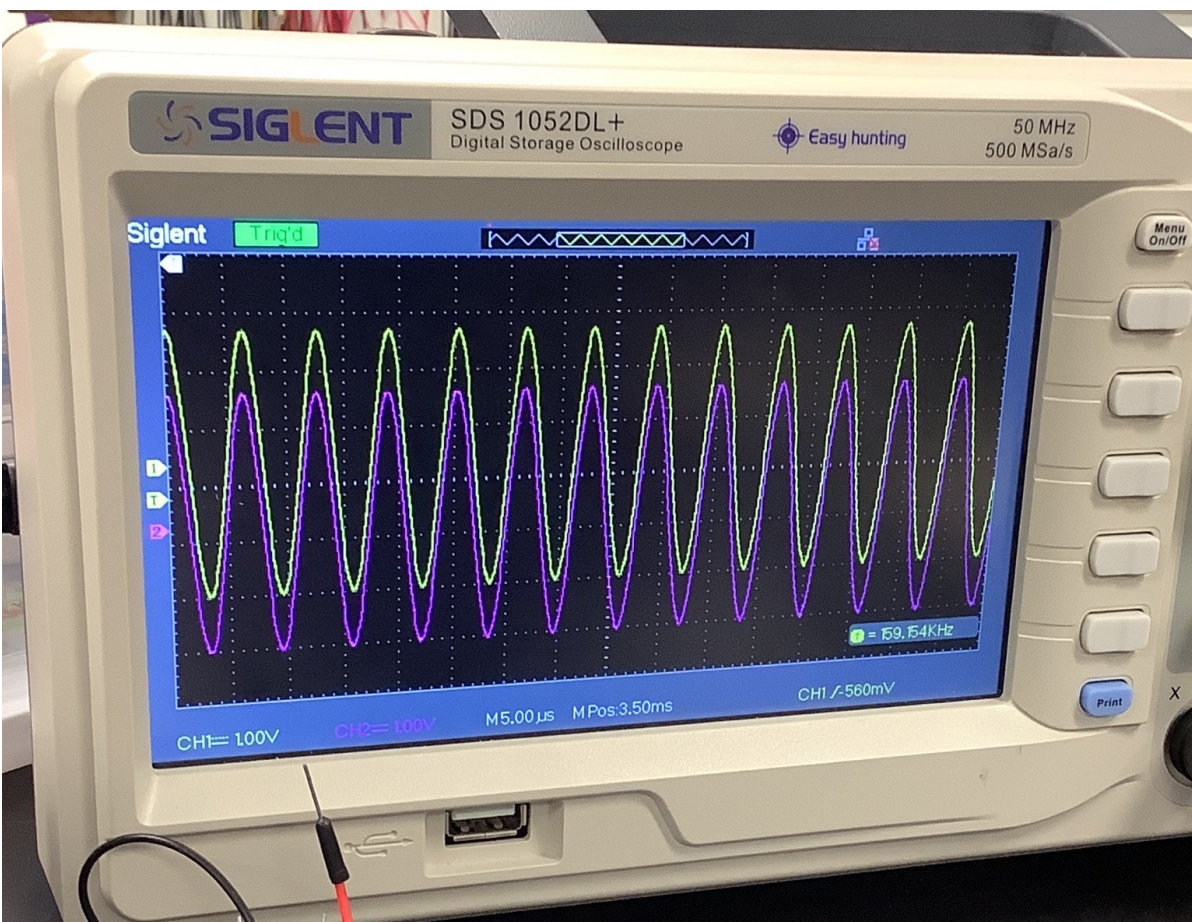Phase shift is close to 0 (slightly negative)




Square Wave:

at $10 \times f_{3dB}$

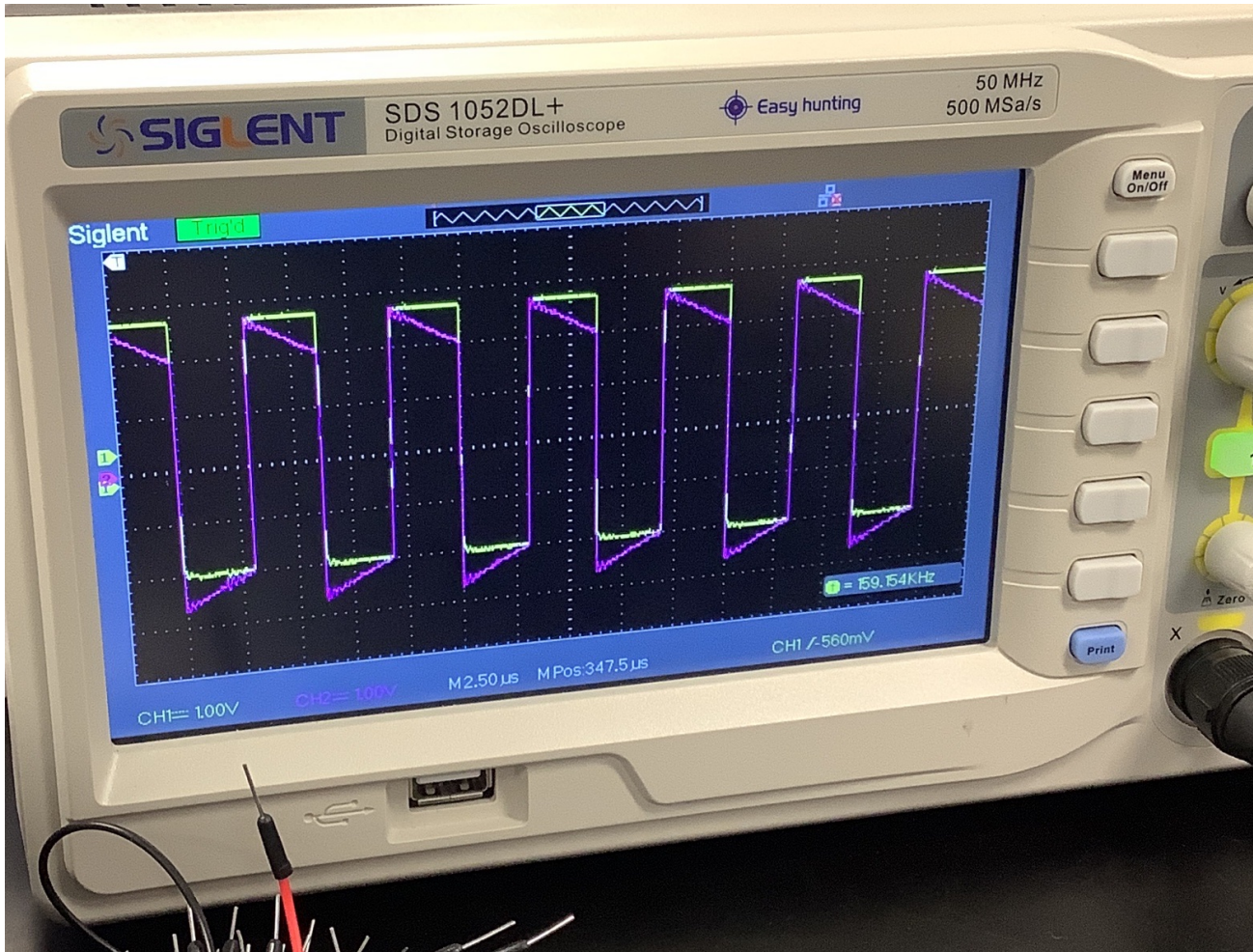


at f_{3dB}

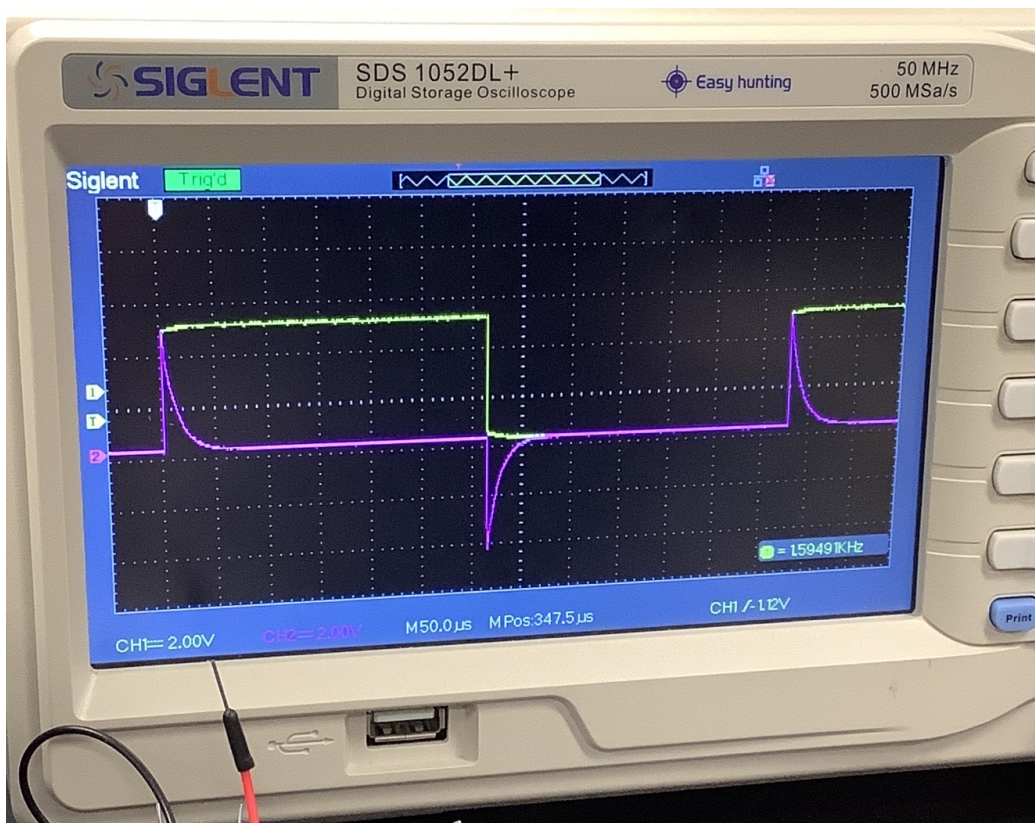

at $\frac{1}{10} f_{3dB}$

The DC component shifts the V_{in} , but does not affect V_{out} .

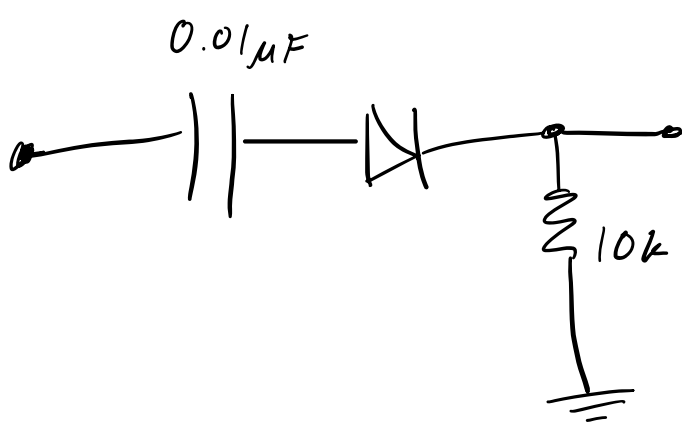With the resistor connected to 5V on the lower end, V_{in} and V_{out} read the same, there is no filtering.



can't go backwards through the diode.


② Low-Pass Filter

$$\frac{1}{10} f_{3dB}$$

$$V_{out} = 2.4(2V) = 4.8V$$

$$V_{in} = 2.4(2V) = 4.8V$$

$$\frac{V_{out}}{V_{in}} = 1$$

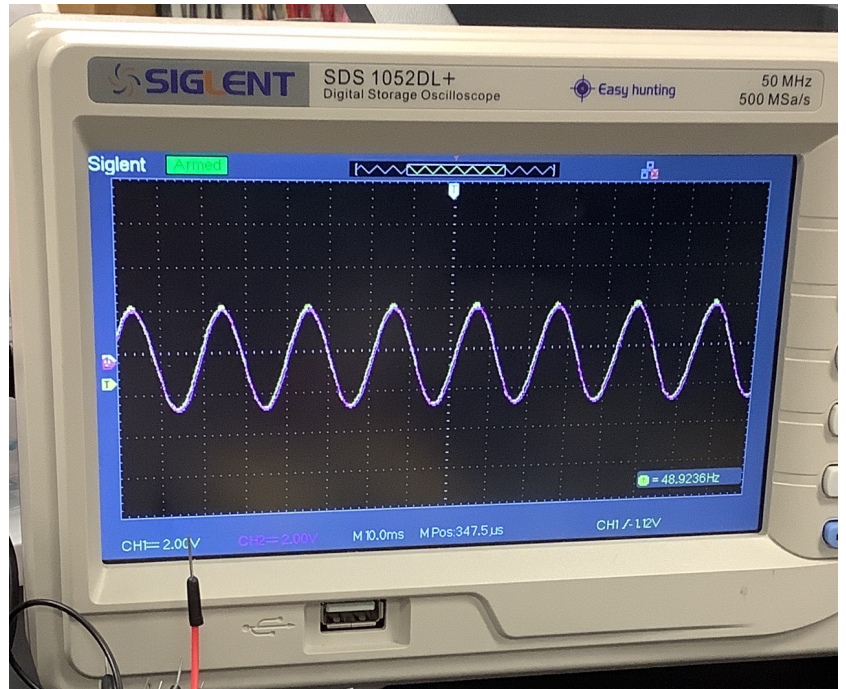


phase shift close to 0 (maybe slightly positive?)

f_{3dB}

$$V_{out} = 2.4 (1V) = 2.4V$$

$$V_{in} = 3.5 (1V) = 3.5V$$
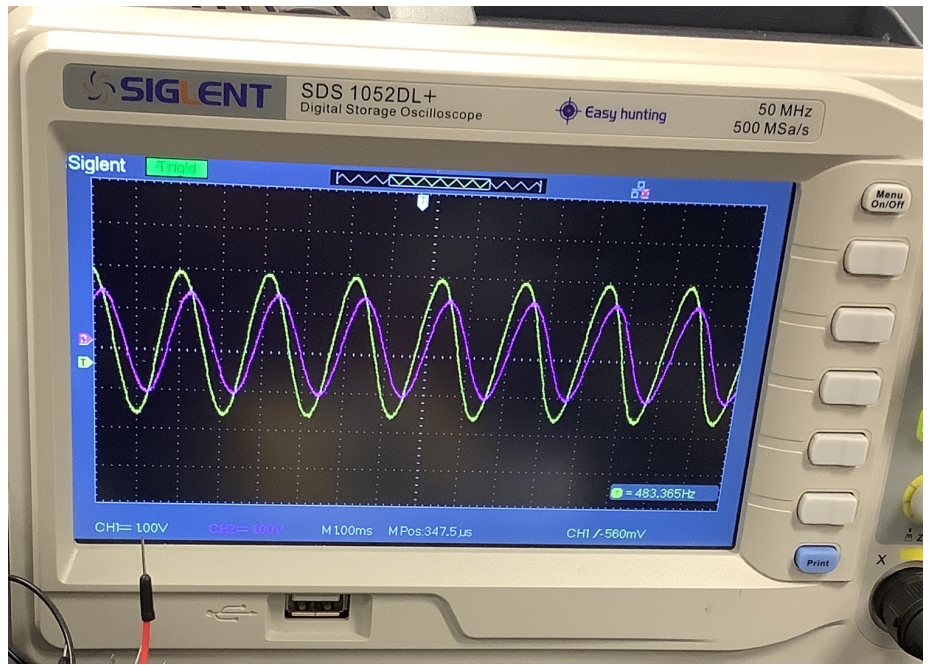
$$\frac{V_{out}}{V_{in}} = \frac{2.4}{3.5}$$




$10 f_{3dB}$


$$V_{out} = 3.6 (100mV) = 0.36V$$

$$V_{in} = 3.1V$$
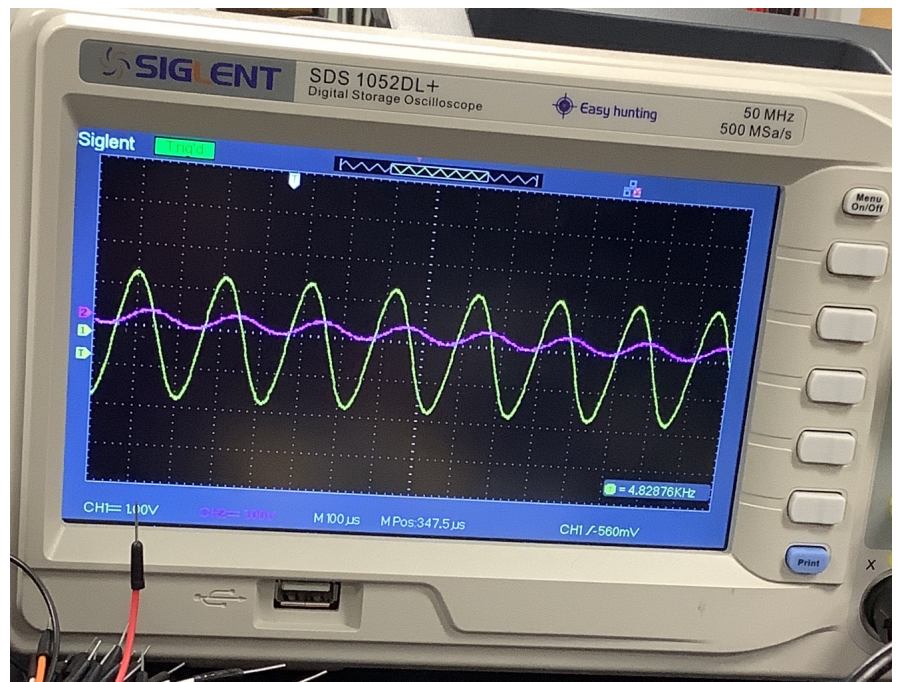
$$\frac{V_{out}}{V_{in}} = \frac{0.36}{3.1}$$



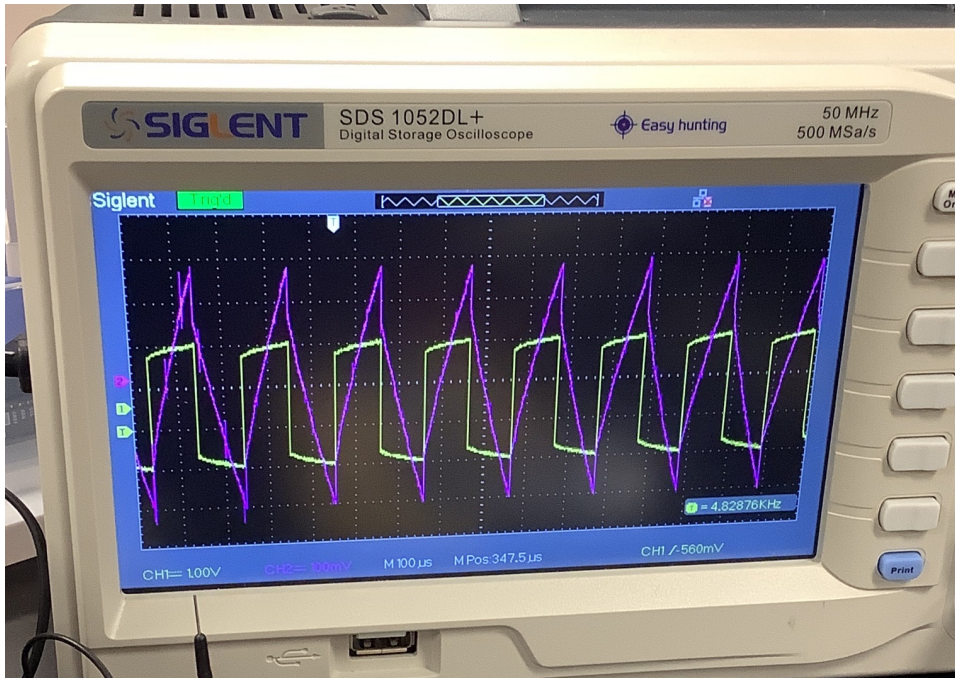This is a low-pass filter, so the lower frequencies go through with almost no change, and higher frequencies are reduced or filtered out.



$10 f_{3dB}$



$\frac{1}{10} f_{3dB}$